

6.002 – Circuits & Electronics – Fall 2007
Problem Set #7 - SOLUTIONS P7.1 and P7.2

Problem 7.1

(A) Circuit: Inductor is connected to the voltage source.
 $i(t) = 1/L \int V dt = V/L t + K$ and since $i(0) = 0 \rightarrow K = 0$
 $\rightarrow i(t) = V/L t$ and $v(t) = 0$ for $0 \leq t \leq T_1$

(B) Circuit: Inductor is connected to the capacitor.
 $v(t) = L di/dt = L d/dt (-C dv/dt) = -LC d^2v/dt^2$
 $\rightarrow d^2v/dt^2 + 1/LC v = 0$
 $v(t) = A \cos [\omega(t-T_1)] + B \sin [\omega(t-T_1)]$ and $\omega = 1/\sqrt{LC}$
 $i(t) = -C dv/dt = CA\omega \sin [\omega(t-T_1)] - CB\omega \cos [\omega(t-T_1)]$
 We know from before at $t=T_1$:
 $v(T_1) = 0 \rightarrow A = 0$ and
 $i(T_1) = V/L T_1 = -CB\omega \rightarrow B = -V/L T_1/(C\omega)$

Therefore:

$v(t) = -T_1/\sqrt{LC} \sin [(t-T_1)/\sqrt{LC}]$ and
 $i(t) = V/L T_1 \cos [(t-T_1)/\sqrt{LC}]$ for $T_1 \leq t \leq T_2$

For T_2 it is required that: $i(T_2) = 0$
 $\rightarrow (T_2-T_1)/\sqrt{LC} = \pi/2 \rightarrow T_2 = \pi/2 \sqrt{LC} + T_1$

(C) Circuit: All three elements are disconnected.
 $v(T_2) = -VT_1/\sqrt{LC}$ and $i(T_2) = 0$
 Therefore:
 $v(t) = -VT_1/\sqrt{LC}$ and
 $i(t) = 0$ for $T_2 \leq t \leq T_3$

(D) Circuit: Inductor is connected to the voltage source. Using information from part (A):
 $i(t) = V/L(t-T_3)$ and
 $v(t) = v(T_3) = v(T_2) = -VT_1/\sqrt{LC}$ for $T_3 \leq t \leq T_4$

(E) Circuit: Inductor is connected to the capacitor.
 Using information from part (B): $d^2v/dt^2 + 1/LC v = 0$
 $v(t) = A \cos [\omega(t-T_4)] + B \sin [\omega(t-T_4)]$ and $\omega = 1/\sqrt{LC}$
 $i(t) = CA\omega \sin [\omega(t-T_4)] - CB\omega \cos [\omega(t-T_4)]$


We know that at T_4 : $v(T_4) = -VT_1/\sqrt{LC} \rightarrow A = -VT_1/\sqrt{LC}$
 $i(T_4) = V/L (T_4-T_3) \rightarrow V/L (T_4-T_3) = -CB\omega \rightarrow B = V/L (T_4-T_3)/(C\omega)$

Therefore:

$v(t) = -VT_1/\sqrt{LC} \cos [(t-T_4)/\sqrt{LC}] - V(T_4-T_3)/\sqrt{LC} \sin [(t-T_4)/\sqrt{LC}]$ and
 $i(t) = -VT_1/L \sin [(t-T_4)/\sqrt{LC}] + V(T_4-T_3)/L \cos [(t-T_4)/\sqrt{LC}]$ for $T_4 \leq t \leq T_5$

We know that at T_5 : $i(T_5) = 0$
 $\rightarrow VT_1/L \sin [(T_5-T_4)/\sqrt{LC}] = V(T_4-T_3)/L \cos [(T_5-T_4)/\sqrt{LC}]$
 $\tan [1/\sqrt{LC}(T_5-T_4)] = (T_4-T_3)/T_1$
 $\rightarrow T_5 = \sqrt{LC} \tan^{-1} [(T_4-T_3)/T_1] + T_4$
 $v(T_5) = -VT_1/\sqrt{LC} \cos [(T_5-T_4)/\sqrt{LC}] - V(T_4-T_3)/\sqrt{LC} \sin [(T_5-T_4)/\sqrt{LC}] \dots$
 $v(T_5) = -V \sqrt{[T_1^2 + (T_4-T_3)^2]}/\sqrt{LC}$

(F)

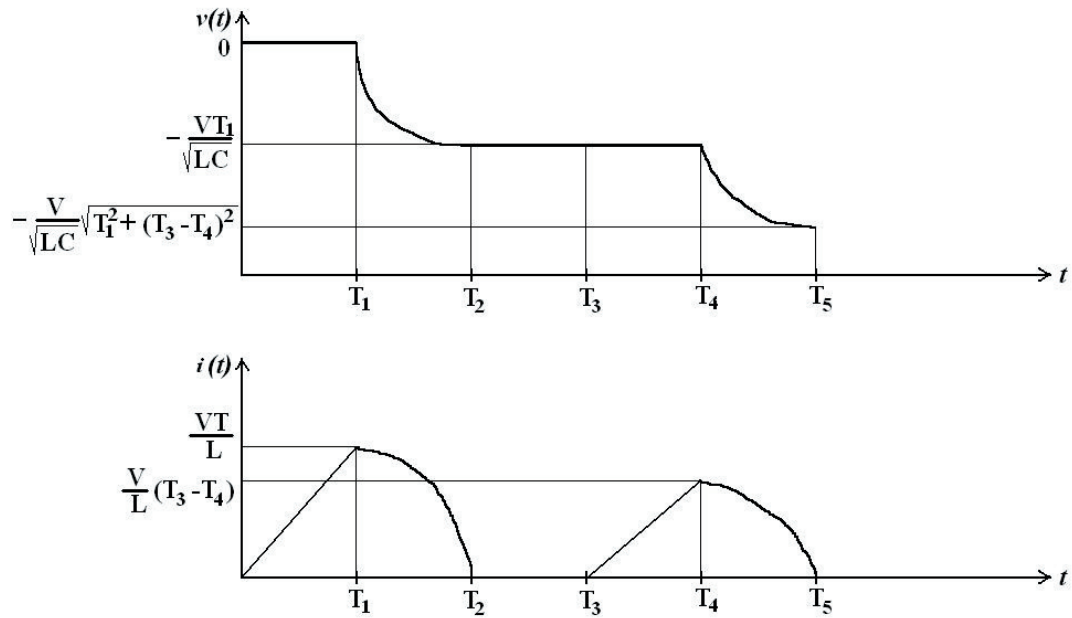

Problem 7.2

- (A) $E_L = 1/2 L i^2(t) = 1/2 L i^2(T_1) = 1/2 L (V/L T_1)^2 = 1/2 V^2 T_1^2 / L$
- (B) $E_L = E_C = 1/2 C v^2(t) = 1/2 C v^2(T_2) \rightarrow 1/2 V^2 T_1^2 / L = 1/2 C v^2(T_2) \rightarrow v(T_2) = -VT_2/\sqrt{LC}$
Negative solution is selected because of the direction of current i .
- (C) $E_L = 1/2 L i^2(T_4) = 1/2 L V^2/L^2 (T_4 - T_3)^2 = 1/2 V^2 (T_4 - T_3)^2 / L$
- (D) $E_L + 1/2 C v^2(T_2) = E_C \rightarrow 1/2 V^2 (T_4 - T_3)^2 / L + 1/2 C v^2(T_2) = 1/2 C v^2(T_5)$
 $v(T_5) = -V/\sqrt{LC} \sqrt{(T_4 - T_3)^2 + T_1^2}$
- (E) From part (D), we see that if $(T_4 - T_3) = T_1$ then: $v(T_5) = -V/\sqrt{LC} \sqrt{(T_1^2 + T_1^2)} = -VT_1/\sqrt{LC} \sqrt{2}$
Hence, after n switching cycles: $v(nT_1) = -VT_1/\sqrt{LC} \sqrt{n} = -VT_1 \sqrt{n/(LC)}$


Solution of PS 8

6.002 Fall 2007

1/10

Exercise 8.1

at time $t=0^+$

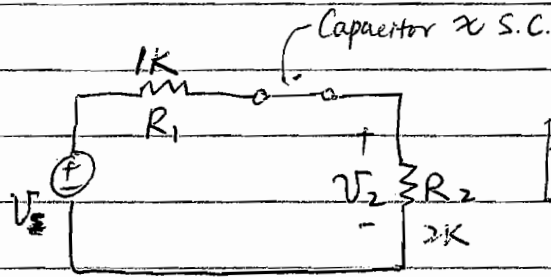


$$V_2(t=0^+) = \frac{R_2}{R_1 + R_2} V_I$$

$$= \frac{2}{3} \cdot 6$$

$$= 4 \text{ (V)}$$

at time $t=\infty$

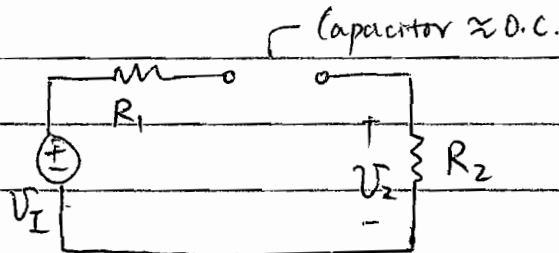


$$V_2(t \rightarrow \infty) = 0$$


time constant

$$\tau = (R_1 + R_2) \cdot C = 3k\Omega \cdot 3\mu F = 9 \text{ ms}$$

$$\therefore V_2(t) = 4 \cdot e^{-t/\tau}$$

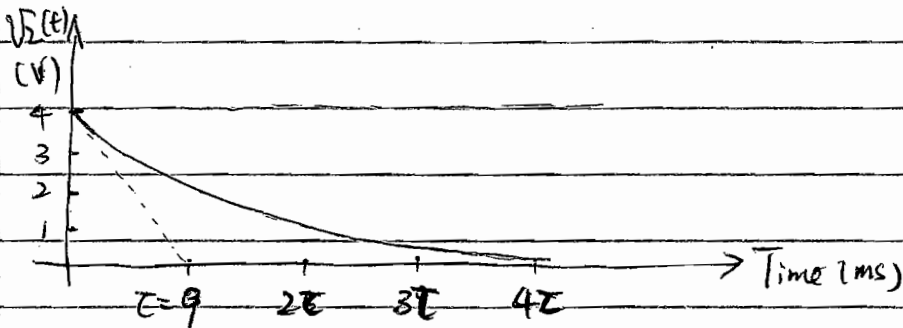

Exercise 8.2.

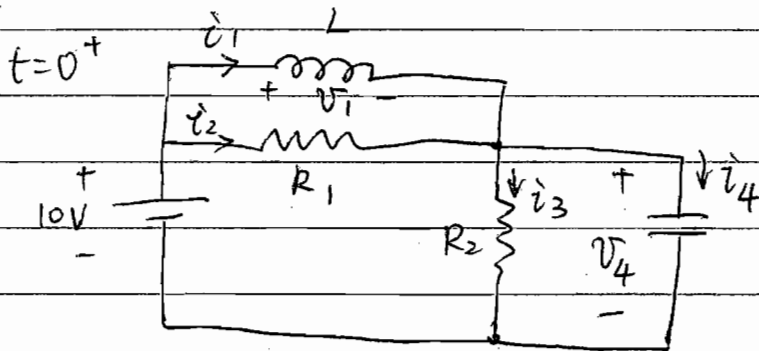

$$R_2 = 15\Omega$$

$$L = 1\text{H}$$

$$C = 0.5\text{F}$$

$$R_1 = 25\Omega$$

From inductor L $i_1(0^+) = i_1(0^-) = 2\text{A}$

From capacitor C $v_4(0^+) = v_4(0^-) = 4\text{V} \Rightarrow i_3(0^+) = \frac{v_4(0^+)}{R_2} = 4\text{A}$

~~From KCL $i_2(0^+) = i_1(0^+)$~~

From KVL $v_1(0^+) = 10 - v_4(0^+) = 6\text{V} \Rightarrow i_2(0^+) = \frac{v_1(0^+)}{R_1} = 3\text{A}$


From KCL $i_4(0^+) = i_1(0^+) + i_2(0^+) - i_3(0^+)$

$$= 2 + 3 - 4$$

$$= 1\text{A}$$

$$\therefore \begin{array}{l} v_1(0^+) = 6\text{V} \quad i_1(0^+) = 2\text{A} \quad i_2(0^+) = 3\text{A} \\ v_4(0^+) = 4\text{V} \quad i_3(0^+) = 4\text{A} \quad i_4(0^+) = 1\text{A} \end{array}$$

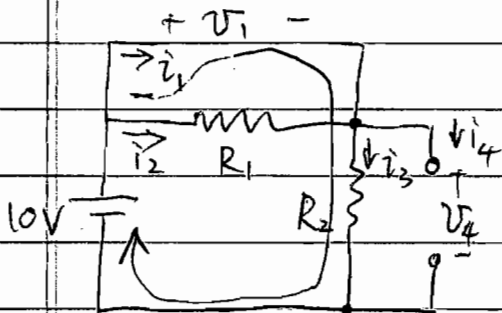$t = \infty$ Inductor $L = \text{S.C.}$ Capacitor $C = \text{O.C.}$




$$i_1(\infty) = i_3(\infty) = \frac{10\text{V}}{R_2} = 10\text{A}$$

$$i_2(\infty) = i_4(\infty) = 0\text{A}$$

$$v_1(\infty) = 0\text{V}$$

$$v_4(\infty) = 10\text{V}$$
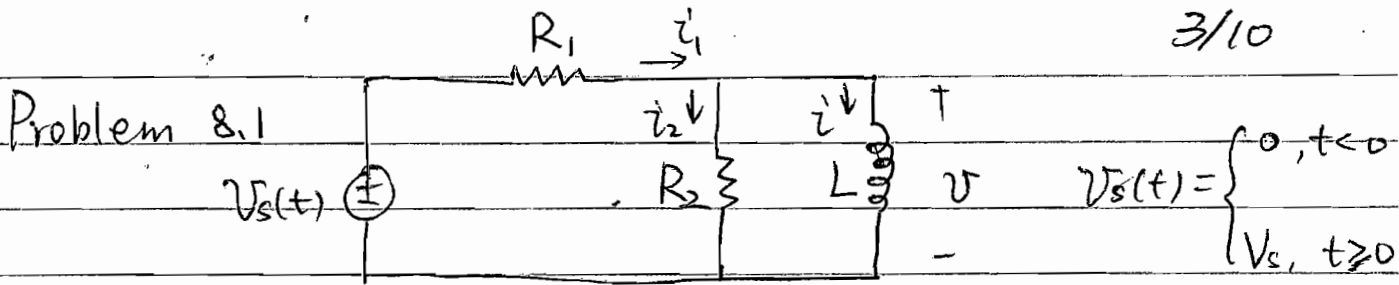
$$\therefore \begin{array}{l} v_1(\infty) = 0\text{V} \quad i_1(\infty) = i_3(\infty) = 10\text{A} \\ v_4(\infty) = 10\text{V} \quad i_2(\infty) = i_4(\infty) = 0\text{A} \end{array}$$



a) From KCL, we have $i_1 = i_2 + i \Rightarrow \frac{V_s - v}{R_1} = \frac{v}{R_2} + i$

From inductor L , we have $v = L \frac{di}{dt}$

Therefore we have differential equation for $v(t)$ & $i(t)$:

$$\begin{cases} \frac{V_s - v(t)}{R_1} = \frac{v(t)}{R_2} + i(t) & \dots (1) \end{cases}$$

$$\begin{cases} v(t) = L \frac{di(t)}{dt} & \dots (2) \end{cases}$$

We can plug (2) into (1) and solve for $i(t)$ first.

Rearrange (1) after plugging (2) into (1), we have,


$$L \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{di(t)}{dt} + i(t) = \frac{V_s}{R_1}$$

Hence the particular solution $i_p(t) = \frac{V_s}{R_1}$
 the homogeneous solution $i_h(t) = A e^{-t/\tau}$ $\tau = L \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$

From the initial condition $i(0^-) = i(0^+) = 0 \Rightarrow A = -\frac{V_s}{R_1}$

$$\therefore i(t) = \frac{V_s}{R_1} (1 - e^{-t/\tau}) \quad t \geq 0$$
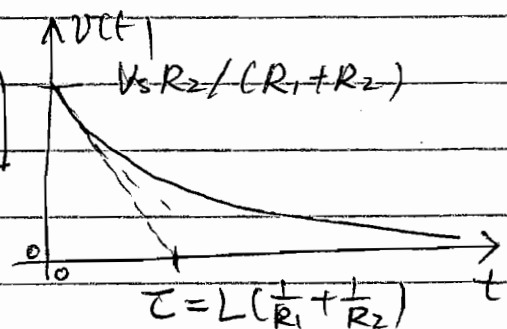
$$\therefore v(t) = L \frac{di(t)}{dt} = \frac{V_s R_2}{R_1 + R_2} e^{-t/\tau} \quad t \geq 0$$




$$b) \text{ Let's say in part a) } V_s(t) = V_{sa}(t) = V_s u_{-1}(t) = \begin{cases} 0, & t < 0 \\ V_s, & t \geq 0 \end{cases}$$

$$\text{in this part, } V_s(t) = V_{sb}(t) = \Lambda u_0(t)$$

$$\therefore V_{sb}(t) = \Lambda u_0(t) = \frac{\Lambda}{V_s} \frac{d(V_{sa}(t))}{dt}$$

\therefore The output $V(t)$ satisfy the similar relation shown in inputs above,
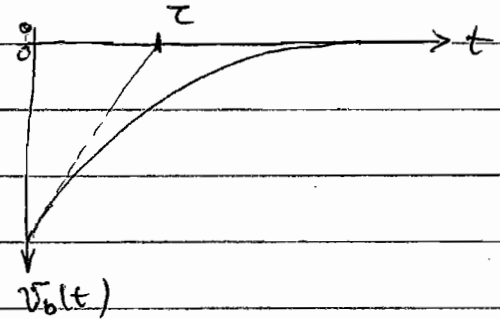
$$\text{i.e., } V_b(t) = \frac{\Lambda}{V_s} \frac{d(V_{sa}(t))}{dt} \quad \left. \begin{array}{l} V(t) \text{ in part b)} \\ V_a(t) = V_s \frac{R_2}{R_1 + R_2} e^{-t/\tau} \\ (V(t) \text{ in part a)} \end{array} \right\} \Rightarrow V_b(t) = -\Lambda \left(\frac{R_2}{R_1 + R_2} \right)^2 \frac{R_1}{L} e^{-t/\tau} \quad t \geq 0$$




$$c) \text{ Similarly, } V_{sc}(t) = M u_{-2}(t)$$


$$\begin{aligned} \therefore V_{sc}(t) &= \frac{M}{V_s} \int V_s u_{-1}(t) dt \\ &= \frac{M}{V_s} \int V_{sa}(t) dt \end{aligned}$$

$$\therefore V_c(t) = \frac{M}{V_s} \int V_{sa}(t) dt \quad \& \quad V_c(0^+) = V_c(0^-) = 0$$

$V_c(t)$ in part c)
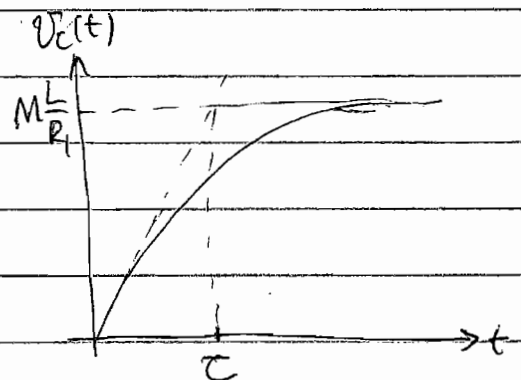
$$\begin{aligned} \therefore V_c(t) &= \frac{M}{V_s} \int V_s \frac{R_2}{R_1 + R_2} e^{-t/\tau} dt \\ &= M \frac{L}{R_1} (1 - e^{-t/\tau}) \end{aligned}$$



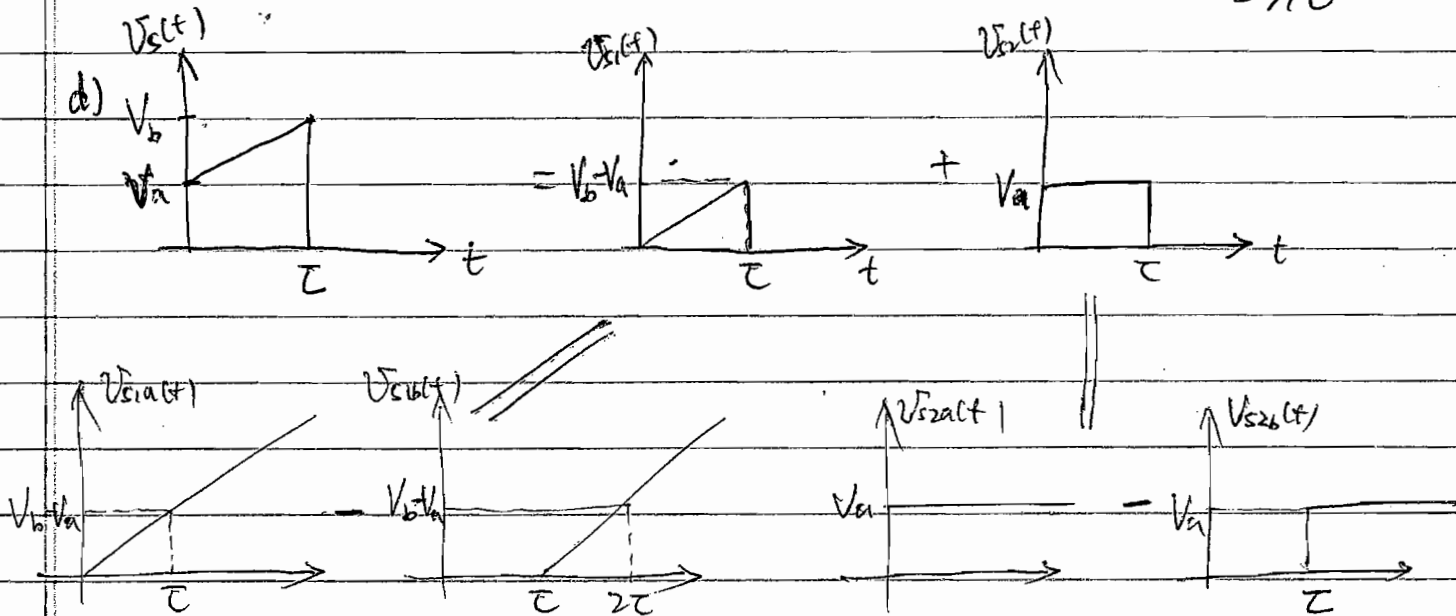

Therefore this input can be decomposed into two ramps and two steps,

$$\begin{aligned}
 V_s(t) &= V_{s1}(t) + V_{s2}(t) = V_{s1a}(t) + V_{s1b}(t) + V_{s2a}(t) + V_{s2b}(t) \\
 &= \frac{V_b - V_a}{\tau} (u_2(t) - u_2(t - \tau)) + V_a (u_1(t) - u_1(t - \tau))
 \end{aligned}$$


e) Using results from a) & c), by superposing response to step and ramp inputs, we can derive $V_e(t)$ ($V(t)$ - in part e)) for $t > 0$,

$$\begin{aligned}
 V_e(t) &= \frac{R_2}{R_1 + R_2} \cdot V_a \cdot (e^{-t/\tau} - e^{-(t-\tau)/\tau}) \\
 &\quad - \left(\frac{L}{R_1} \right) \cdot \frac{V_b - V_a}{\tau} \cdot (e^{-t/\tau} - e^{-(t-\tau)/\tau}) \\
 &= \left(\frac{R_2 V_a}{R_1 + R_2} - \frac{L(V_b - V_a)}{R_1 \tau} \right) \cdot (e^{-t/\tau} - e^{-(t-\tau)/\tau})
 \end{aligned}$$

$\therefore \tau = L \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$ from part a)

\therefore we can further simplify $V_e(t) = \frac{R_2}{R_1 + R_2} \cdot (2V_a - V_b) \cdot (e^{-t/\tau} - e^{-(t-\tau)/\tau})$

Problem 8.2

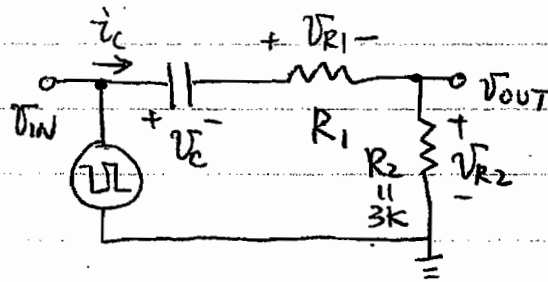

a) When $v_{in} = V$, from KVL, we have, $V = v_c(t) + v_{R1}(t) + v_{R2}(t)$

$$\therefore v_{R1}(t) = R_1 \cdot i_c(t), \quad v_{R2}(t) = R_2 \cdot i_c(t), \quad \text{and } i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\therefore V = v_c(t) + (R_1 + R_2) \cdot C \frac{dv_c(t)}{dt}$$

$$\Rightarrow V = v_c(t) + \tau \cdot \frac{dv_c(t)}{dt} \quad \text{where } \tau = (R_1 + R_2)C$$

If define $t=0$ when source v_{in} jumps from $-V$ to V , then we have

$$\tau \cdot \frac{dv_c(t)}{dt} + v_c(t) = V \quad \& \quad v_c(t=0^-) = -V$$

Similarly, we define $t'=0$ when source v_{in} jumps from V to $-V$, then

$$\text{we have } \tau \cdot \frac{dv_c(t')}{dt'} + v_c(t') = -V \quad \& \quad v_c(t'=0^-) = V$$

Solve equations above, we have


$$v_c(t) = \begin{cases} V - 2V e^{-t/\tau} & v_{in} = V \\ -V + 2V e^{-t'/\tau} & v_{in} = -V \end{cases}$$

$$b) \therefore i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\therefore i_c(t) = \begin{cases} \frac{2VC}{\tau} e^{-t/\tau} & v_{in} = V \text{ (or, } \frac{2V}{R_1 + R_2} e^{-t/\tau}) \\ -\frac{2VC}{\tau} e^{-t'/\tau} & v_{in} = -V \text{ (or, } \frac{-2V}{R_1 + R_2} e^{-t'/\tau}) \end{cases}$$

$$c) \therefore v_{R2}(t) = R_2 \cdot i_c(t)$$
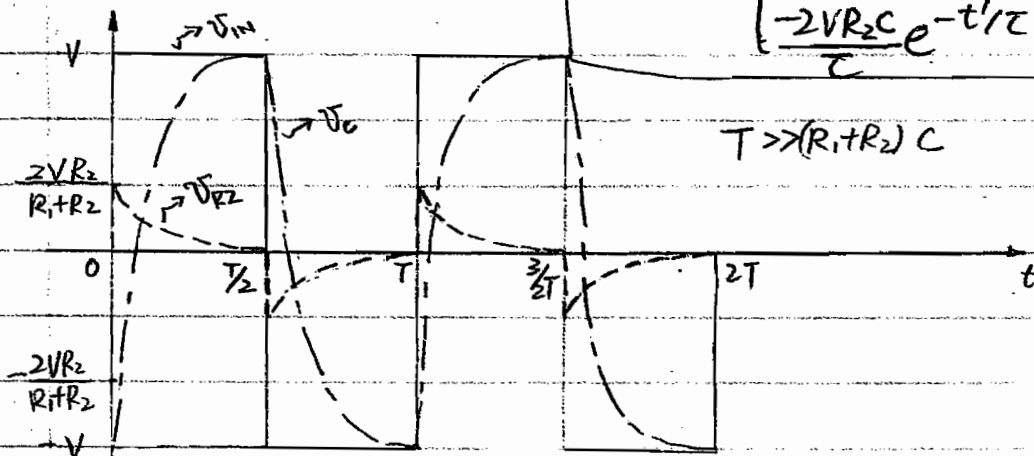
$$\therefore v_{R2}(t) = \begin{cases} \frac{2VR_2C}{\tau} e^{-t/\tau} & v_{in} = V \text{ (or, } \frac{2VR_2}{R_1 + R_2} e^{-t/\tau}) \\ -\frac{2VR_2C}{\tau} e^{-t'/\tau} & v_{in} = -V \text{ (or, } \frac{2VR_2}{R_1 + R_2} e^{-t'/\tau}) \end{cases}$$



Notice that

$$t' = t - T/2$$

where $T = \frac{1}{f}$

d) For V_{R2} , we have $V_{R2}(0^+) = 206 \text{ mV}$, $V_{R2}(1.1 \text{ ms}) = 10.3 \text{ mV} = 0.05 \times V_{R2}(0^+)$


$\therefore 3\tau = 1.1 \text{ ms} \Rightarrow \tau \approx 0.367 \text{ ms}$ (Don't need to be so accurate actually. 0.3 ms is fine.)

e) Before the input switches from positive to negative, $V_C = 1.19 \text{ V} = V_{IN}$. After the input switches to negative, V_C keeps the same as 1.19 V while $V_{IN} = -1.14 \text{ V}$.

So we have, $\frac{-1.19 - (-1.14)}{R_1 + R_2} = \frac{-1.90 \times 10^{-3}}{R_2} \Rightarrow R_1 \approx 34 \text{ k}$ (given $R_2 = 3 \text{ k}$)

f) $\tau = (R_1 + R_2) \cdot C \Rightarrow C = \frac{\tau}{R_1 + R_2} = \frac{0.367 \text{ ms}}{34 \text{ k} + 3 \text{ k}} \approx 9.9 \text{ nF} = 9.9 \times 10^{-9} \text{ F}$

problem 8.3.

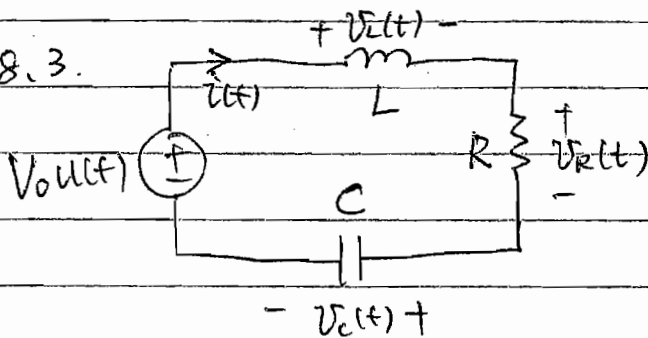

a) $V_C(0) = 0$, because capacitor behaves like short circuit @ $t=0$

$i(0) = 0$, because inductor behaves like open circuit @ $t=0$

$\therefore V_R(0) = i(0) \cdot R = 0$

$V_L(0) = V_0 u(0) - V_R(0) - V_C(0) = V_0$

$\therefore V_L = L \frac{di}{dt}$

$\therefore \left. \frac{di}{dt} \right|_{t=0} = \frac{V_L(0)}{L} = \frac{V_0}{L}$

b) Because capacitor behaves like open circuit @ $t=\infty$, $\therefore i(t=\infty) = 0$

b) $V_C(t) = V_0(1 - \cos(\omega_0 t))$ $\omega_0 = \frac{1}{\sqrt{LC}}$, $t > 0$

$i(t) = \sqrt{\frac{C}{L}} V_0 \sin(\omega_0 t)$

d) From KVL, we have, $V_0 = V_L(t) + V_R(t) + V_C(t)$

$$= L \frac{di(t)}{dt} + i(t) \cdot R + \frac{1}{C} \int i(t) dt$$

$$\Rightarrow 0 = L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t)$$

$$\Rightarrow \boxed{\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0}$$

$$\textcircled{a} \frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0 \Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\therefore s = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \therefore \alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= -\alpha \pm j\omega_d \quad \therefore \omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad (\omega_0 > \alpha)$$

$$i(t) = e^{-\alpha t} (A \cos(\omega_d t) + B \sin(\omega_d t))$$

$$\because i(0) = 0 \quad \therefore A = 0$$

$$\therefore i(t) = B e^{-\alpha t} \sin(\omega_d t)$$

$$\frac{di(t)}{dt} = -\alpha B e^{-\alpha t} \sin(\omega_d t) + B e^{-\alpha t} \cdot \omega_d \cos(\omega_d t)$$


$$\therefore \left. \frac{di(t)}{dt} \right|_{t=0} = \frac{V_0}{L} \Rightarrow B \omega_d = \frac{V_0}{L} \Rightarrow B = \frac{V_0}{\omega_d L}$$

$$\therefore i(t) = \frac{V_0}{\omega_d L} e^{-\alpha t} \sin(\omega_d t) = I e^{-\alpha t} \sin(\omega t + \phi)$$

$$\text{Where } I = \frac{V_0}{L \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}, \omega = \omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}, \phi = 0, \alpha = \frac{R}{2L}$$

9/10

20k sampling rate, 5ms duration

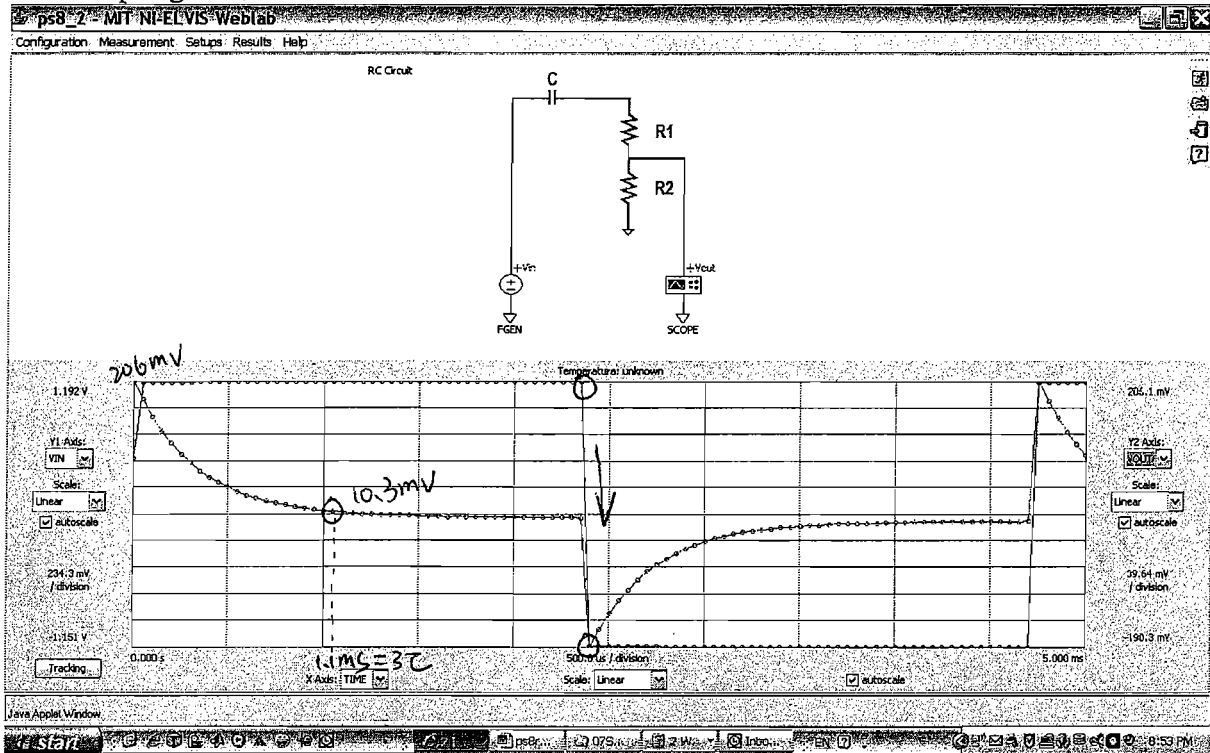

time constant is about 0.367 ms

R1 is about 34 Kohm

C is about $9.9 \mu\text{F} = 9.9 \times 10^{-9} \text{F}$

TIME, VIN, VOUT s, V, V	TIME, VIN, VOUT s, V, V
0, 512.032192234953e-3, 206.099181203987e-3	2.95e-3, -1.14805397227293, -38.0029255723793e-3
50e-6, 1.182187934163, 179.048278663754e-3	3e-3, -1.14837600601138, -32.8503763883594e-3
100e-6, 1.18379811410142, 153.607551136429e-3	3.05e-3, -1.14869803974978, -28.9859644501187e-3
150e-6, 1.18476422207144, 132.353274082149e-3	3.1e-3, -1.14869803974978, -25.4435868021231e-3
200e-6, 1.18605236603962, 113.67527424834e-3	3.15e-3, -1.14902007348815, -21.901209117733e-3
250e-6, 1.18701847402186, 97.8955856072151e-3	3.2e-3, -1.14934210722647, -19.3249344152606e-3
300e-6, 1.18766254601292, 84.6921732706709e-3	3.25e-3, -1.14966414096476, -17.7147627163963e-3
350e-6, 1.18830661800632, 72.7768991940769e-3	3.3e-3, -1.149986174703, -15.4605223252762e-3
400e-6, 1.18862865400389, 62.7938320656817e-3	3.35e-3, -1.14966414096476, -13.8503506082418e-3
450e-6, 1.18895069000205, 54.7429717032384e-3	3.4e-3, -1.14966414096476, -12.2401788836208e-3
500e-6, 1.1895947620001, 47.9802491530912e-3	3.45e-3, -1.14934210722647, -11.2740758452027e-3
550e-6, 1.18927272600078, 41.2175267430959e-3	3.5e-3, -1.14966414096476, -9.66390410842352e-3
600e-6, 1.19023883400048, 36.0649764291233e-3	3.55e-3, -1.149986174703, -9.0198354115813e-3
650e-6, 1.1908829060032, 31.234460583027e-3	3.6e-3, -1.149986174703, -8.37576671352073e-3
700e-6, 1.19023883400048, 27.6920823407948e-3	3.65e-3, -1.15030820844121, -7.08762931374214e-3
750e-6, 1.1908829060032, 24.1497041364478e-3	3.7e-3, -1.149986174703, -6.76559496303509e-3
800e-6, 1.1908829060032, 21.5734291024798e-3	3.75e-3, -1.149986174703, -6.44356061202293e-3
850e-6, 1.19056087000155, 18.9971540884594e-3	3.8e-3, -1.149986174703, -5.79949190908297e-3
900e-6, 1.19120494200543, 16.4208790943484e-3	3.85e-3, -1.15063024217937, -5.79949190908297e-3
950e-6, 1.19120494200543, 14.8107072331223e-3	3.9e-3, -1.149986174703, -5.79949190908297e-3
1e-3, 1.1908829060032, 12.556466640284e-3	3.95e-3, -1.149986174703, -5.15542320492167e-3
1.05e-3, 1.19152697800825, 11.5903635339193e-3	4e-3, -1.149986174703, -4.51135449953844e-3
1.1e-3, 1.1908829060032, 10.3022260629046e-3	4.05e-3, -1.15063024217937, -4.51135449953844e-3
1.15e-3, 1.19120494200543, 9.33612296288898e-3	4.1e-3, -1.14966414096476, -3.86728579293267e-3
1.2e-3, 1.1908829060032, 8.04798550052501e-3	4.15e-3, -1.15063024217937, -3.86728579293267e-3
1.25e-3, 1.19120494200543, 8.04798550052501e-3	4.2e-3, -1.149986174703, -3.86728579293267e-3
1.3e-3, 1.19056087000155, 7.08188240699204e-3	4.25e-3, -1.149986174703, -3.86728579293267e-3
1.35e-3, 1.19184901401164, 6.75984804309779e-3	4.3e-3, -1.14966414096476, -3.86728579293267e-3
1.4e-3, 1.1908829060032, 6.43781367951178e-3	4.35e-3, -1.149986174703, -3.22321708510377e-3
1.45e-3, 1.1908829060032, 6.11577931623395e-3	4.4e-3, -1.15063024217937, -2.90118273073046e-3
1.5e-3, 1.19120494200543, 5.14967622824875e-3	4.45e-3, -1.15030820844121, -2.90118273073046e-3
1.55e-3, 1.1908829060032, 4.82764186620286e-3	4.5e-3, -1.14966414096476, -3.54525143917115e-3
1.6e-3, 1.1908829060032, 4.82764186620286e-3	4.55e-3, -1.15030820844121, -3.22321708510377e-3
1.65e-3, 1.19056087000155, 4.18357314303441e-3	4.6e-3, -1.149986174703, -3.22321708510377e-3
1.7e-3, 1.19120494200543, 4.50560750446477e-3	4.65e-3, -1.149986174703, -2.90118273073046e-3
1.75e-3, 1.19152697800825, 4.18357314303441e-3	4.7e-3, -1.14966414096476, -2.57914837605114e-3
1.8e-3, 1.19120494200543, 4.18357314303441e-3	4.75e-3, 1.1805777542391, 205.777146635314e-3
1.85e-3, 1.19184901401164, 4.18357314303441e-3	4.8e-3, 1.18283200613662, 176.472002360183e-3
1.9e-3, 1.19120494200543, 3.21747006058892e-3	4.85e-3, 1.18412015009085, 151.997378580386e-3
1.95e-3, 1.19184901401164, 3.53950442109656e-3	4.9e-3, 1.18508625806262, 130.743101638189e-3
2e-3, 1.19120494200543, 3.53950442109656e-3	4.95e-3, 1.18605236603962, 112.065101901535e-3
2.05e-3, 1.19152697800825, 3.53950442109656e-3	5e-3, 1.18701847402186, 96.2854133415102e-3
2.1e-3, 1.19184901401164, 3.21747006058892e-3	
2.15e-3, 1.19120494200543, 3.53950442109656e-3	
2.2e-3, 1.19152697800825, 3.21747006058892e-3	
2.25e-3, 1.19184901401164, 3.21747006058892e-3	
2.3e-3, 1.19152697800825, 3.53950442109656e-3	
2.35e-3, 1.19217105001562, 2.8954357003887e-3	
2.4e-3, -1.13968109505891, -190.325127692427e-3	
2.45e-3, -1.14161329749541, -163.596289087623e-3	
2.5e-3, -1.14257939871309, -139.765756723489e-3	
2.55e-3, -1.14386753366942, -120.765736601765e-3	
2.6e-3, -1.14515566862509, -104.664023875416e-3	
2.65e-3, -1.14579973610267, -89.8504475438291e-3	
2.7e-3, -1.1461217698414, -77.2911106152867e-3	
2.75e-3, -1.1461217698414, -67.3080476154098e-3	
2.8e-3, -1.14708787105735, -58.613121548975e-3	
2.85e-3, -1.14740990479592, -50.2402295793757e-3	
2.9e-3, -1.14740990479592, -44.4436119452075e-3	